

CSE 4207 CT 4 Assignment
Roll No: 1903073

Assignment Problem:

Category: C

Word Size = 6

ALU Operations = SHR, XNOR

Solution:

Video:

Have you uploaded the video?	YES
Check List 1: Have you explained the design using testbenches to prove that your circuit is working correctly and giving correct results?	YES
Check List 2: Have you shown full synthesis results showing all the required info including RTL Synthesis, RTL Floorplan, RTL Power Analysis, GDS and Heatmap (for details, see assignment template doc)?	YES
NB: Failing to upload video will cause heavy point penalty (5-6 Marks)	
NB: Failing to add any required info will cause point penalty (1-2 Marks)	

HDL Code:

Check List: Have you added all the modules written in verilog including ALU, ALU_OP1, ALU_OP2, CONTROLLER, TOP, TOP_TESTBENCH, ALU_TESTBENCH, CONTROLLER_TESTBENCH?	YES
NB: Failing to add any required info will cause point penalty (1-2 Marks)	

Google drive link of all the code files:

📁 19CT4Assignment_Code_Files_1903073

alu.v

```
module alu
(
    input wire [5:0] alu_in1, alu_in2,
    input wire [1:0] alu_op,
    output wire [5:0] alu_out,
    output wire alu_flag
);

reg [5:0] result;
```

```

wire [5:0] SHR, XNOR;

ALU_SHR_Nbit SHR1
(
    .A(alu_in1),
    .B(alu_in2),
    .R(SHR)
);

XNOR_Nbit XNOR1
(
    .A(alu_in1),
    .B(alu_in2),
    .R(XNOR)
);

always @(*)
begin
    case (alu_op)
        2'b00: result = SHR; // Right Shift
        2'b01: result = XNOR; // XNOR
        default: result = 6'b0;
    endcase
end

assign alu_out = result;
assign alu_flag = (result > 6'b0);

endmodule

```

alu_op1.v

```

module ALU_SHR_Nbit
(
    input wire [5:0] A,
    input wire [5:0] B,
    output wire [5:0] R
);

    assign R = A >> B;

endmodule

```

alu_op2.v

```

module XNOR_Nbit
(
    input wire [5:0] A,B,
    output wire [5:0] R
);

```

```
assign R = ~(A ^ B);
endmodule
```

controller.v

```
module alu_controller
(
    input wire clk, reset, start,
    input wire [5:0] a, b,
    input wire [1:0] op,

    input wire [5:0] alu_out,
    input wire alu_flag,
    output wire [5:0] alu_in1, alu_in2,
    output wire [1:0] alu_op,

    output reg [5:0] result,
    output reg flag
);

reg [2:0] pstate, nstate;

parameter [2:0] START = 3'b000,
                ONE = 3'b001,
                TWO = 3'b010,
                THREE = 3'b011,
                FINISH = 3'b100;

// Memory
always @(posedge clk, posedge reset)
begin : PSR
    if (reset)
        begin
            pstate <= START;
        end
    else
        begin
            pstate <= nstate;
        end
    end
end

// Next State Logic
always @(*)
begin: NSOL
    // Monitor output
    if(pstate == START)
        $monitor("pstate = START -> clk = %b, reset = %b, start = %b, a = %d, b = %d, op = %b, result = %d, flag = %b\n*****\n", clk, reset, start, a, b, op, result, flag);
    end
end
```

```

        else if(pstate == ONE)
            $monitor("pstate = ONE -> clk = %b, reset = %b, start =
            %b, a = %d, b = %d, op = %b, result = %d, flag =
            %b\n*****\n", clk, reset, start, a,
            b, op, result, flag);
        else if(pstate == TWO)
            $monitor("pstate = TWO -> clk = %b, reset = %b, start =
            %b, a = %d, b = %d, op = %b, result = %d, flag =
            %b\n*****\n", clk, reset, start, a,
            b, op, result, flag);
        else if(pstate == THREE)
            $monitor("pstate = THREE -> clk = %b, reset = %b, start =
            %b, a = %d, b = %d, op = %b, result = %d, flag =
            %b\n*****\n", clk, reset, start, a,
            b, op, result, flag);
        else if(pstate == FINISH)
            $monitor("pstate = FINISH -> clk = %b, reset = %b, start =
            %b, a = %d, b = %d, op = %b, result = %d, flag =
            %b\n*****\n", clk, reset, start, a,
            b, op, result, flag);

        nstate = pstate;

// Next State Logic and Output Logic
begin: NSL
case (pstate)
    START:
        begin
            if (start)
                nstate = ONE;
        end

    ONE:
        begin
            nstate = TWO;
        end

    TWO:
        begin
            nstate = THREE;
        end

    THREE:
        begin
            nstate = FINISH;
        end

    FINISH:
        begin
            nstate = FINISH;
        end
end

```

```

        default:
            nstate = START;
        endcase
    end
begin: OL
    result = 6'b0;
    flag = 0;
    case (pstate)
        START:
            begin
                result = 6'b0;
                flag = 0;
            end

        ONE:
            begin
                result = alu_out;
                flag = alu_flag;
            end

        TWO:
            begin
                result = alu_out;
                flag = alu_flag;
            end

        THREE:
            begin
                result = alu_out;
                flag = alu_flag;
            end

        FINISH:
            begin
                result = alu_out;
                flag = alu_flag;
            end
        default:
            nstate = START;
    endcase
end
end

assign alu_in1 = a;
assign alu_in2 = b;
assign alu_op = op;

endmodule

```

top.v

```

module alu_top
(
    input wire clk, reset, start,
    input wire [5:0] a, b,
    input wire [1:0] op,
    output wire [5:0] result,
    output wire flag
);

wire [5:0] alu_in1, alu_in2;
wire [1:0] alu_op;
wire [5:0] alu_out;
wire alu_flag;

alu_controller controller1
(
    .clk(clk),
    .reset(reset),
    .start(start),
    .a(a),
    .b(b),
    .op(op),
    .alu_in1(alu_in1),
    .alu_in2(alu_in2),
    .alu_op(alu_op),
    .alu_out(alu_out),
    .alu_flag(alu_flag),
    .result(result),
    .flag(flag)
);

alu datapath1
(
    .alu_in1(alu_in1),
    .alu_in2(alu_in2),
    .alu_op(alu_op),
    .alu_out(alu_out),
    .alu_flag(alu_flag)
);

endmodule

```

top_testbench.v

```

`timescale 1ns/1ns

module alu_top_tb;

reg clk, reset, start;
reg [5:0] a, b;
reg [1:0] op;

```

```

wire [5:0] result;
wire flag;

alu_top top1
(
    .clk(clk),
    .reset(reset),
    .start(start),
    .a(a),
    .b(b),
    .op(op),
    .result(result),
    .flag(flag)
);

initial begin

    clk = 0;
    forever #5 clk = ~clk; // Toggle clk every 5 time units
end

initial begin
    $dumpfile("alu_top.vcd");
    $dumpvars(0, alu_top_tb);

    clk <= 0;
    reset <= 0;
    start <= 0;
    a <= 0;
    b <= 0;
    op <= 0;

    @(negedge clk);
    reset <= 1;

    @(negedge clk);
    reset <= 0;
    start <= 1;
    a <= 6'b111100; // 60
    b <= 6'b000010; // 2
    op <= 2'b00; // Right Shift: 111100 >> 2 = 001111 (15, flag =
1)
    #20;

    a <= 6'b000000;
    b <= 6'b000001;
    op <= 2'b00; // Right Shift: 000000 >> 1 = 000000 (0, flag =
0)
    #20;

    a <= 6'b101010; // 42

```

```

    b <= 6'b110011; // 51
    op <= 2'b01; // XNOR: ~(101010 ^ 110011) = ~011001 = 100110
(38, flag = 1)
    #20;

    $finish();
end

endmodule

```

alu_testbench.v

```

`timescale 1ns / 1ps

module alu_tb;

    // Inputs
    reg [5:0] alu_in1;
    reg [5:0] alu_in2;
    reg [1:0] alu_op;

    // Outputs
    wire [5:0] alu_out;
    wire alu_flag;

    // Instantiate the Unit Under Test (UUT)
    alu uut (
        .alu_in1(alu_in1),
        .alu_in2(alu_in2),
        .alu_op(alu_op),
        .alu_out(alu_out),
        .alu_flag(alu_flag)
    );

    initial begin
        $dumpfile("alu_tb.vcd");
        $dumpvars(0, alu_tb);
    end

```



```

// Initialize Inputs
alu_in1 = 6'b0;
alu_in2 = 6'b0;
alu_op = 2'b0;

// Wait for global reset
#100;

// Test Case 1: Right Shift (alu_op = 00)
alu_op = 2'b00;
alu_in1 = 6'b110000; // 48 in decimal
alu_in2 = 6'b000010; // Shift by 2
#20;
$display("Test 1 - SHR: in1=%b, in2=%b, out=%b, flag=%b",
alu_in1, alu_in2, alu_out, alu_flag);

// Test Case 2: Right Shift (alu_op = 00)
alu_in1 = 6'b001100; // 12 in decimal
alu_in2 = 6'b000001; // Shift by 1
#20;
$display("Test 2 - SHR: in1=%b, in2=%b, out=%b, flag=%b",
alu_in1, alu_in2, alu_out, alu_flag);

// Test Case 3: XNOR (alu_op = 01)
alu_op = 2'b01;
alu_in1 = 6'b101010;
alu_in2 = 6'b110011;
#20;
$display("Test 3 - XNOR: in1=%b, in2=%b, out=%b, flag=%b",
alu_in1, alu_in2, alu_out, alu_flag);

// Test Case 4: XNOR (alu_op = 01)
alu_in1 = 6'b111111;
alu_in2 = 6'b111111;
#20;
$display("Test 4 - XNOR: in1=%b, in2=%b, out=%b, flag=%b",

```

```

alu_in1, alu_in2, alu_out, alu_flag);

    // Test Case 5: Default case (alu_op = 10 or 11)
    alu_op = 2'b10;
    alu_in1 = 6'b101010;
    alu_in2 = 6'b110011;
    #20;
    $display("Test 5 - Default: in1=%b, in2=%b, out=%b,
flag=%b", alu_in1, alu_in2, alu_out, alu_flag);

    // Test Case 6: Zero output test
    alu_op = 2'b01; // XNOR
    alu_in1 = 6'b000000;
    alu_in2 = 6'b000000;
    #20;
    $display("Test 6 - XNOR Zero: in1=%b, in2=%b, out=%b,
flag=%b", alu_in1, alu_in2, alu_out, alu_flag);

    // Finish simulation
    #20;
    $finish;
end

endmodule

```

controller_testbench.v

```

`timescale 1ns / 1ps
module alu_controller_tb;

    reg clk, reset, start;
    reg [5:0] a, b;
    reg [1:0] op;
    reg [5:0] alu_out;
    reg alu_flag;
    wire [5:0] alu_in1, alu_in2;
    wire [1:0] alu_op;
    wire [5:0] result;
    wire flag;

    alu_controller dut (
        .clk(clk),
        .reset(reset),
        .start(start),
        .a(a),
        .b(b),
        .op(op),
        .alu_out(alu_out),
        .alu_flag(alu_flag),
        .alu_in1(alu_in1),
        .alu_in2(alu_in2),
        .alu_op(alu_op),
        .result(result),
        .flag(flag)
    );

    initial begin
        $dumpfile("alu_controller.vcd");
        $dumpvars(0, alu_controller_tb);

        clk = 0;
    end

```

```
        forever #5 clk = ~clk;
    end
```

```
initial begin
```

```
    reset = 0;
    start = 0;
    a = 6'b000000;
    b = 6'b000000;
    op = 2'b00;
    alu_out = 6'b000000;
    alu_flag = 0;
```

```
    #10;
    reset = 1;
```

```
    #10;
    reset = 0;
    start = 1;
    a = 6'b111100;
    b = 6'b000010;
    op = 2'b00;
    alu_out = 6'b001111;
    alu_flag = 1;
```

```
    #15;
    a = 6'b000000;
    b = 6'b000001;
    op = 2'b00;
    alu_out = 6'b000000;
    alu_flag = 0;
```

```

        #10;

        a = 6'b101010;
        b = 6'b110011;
        op = 2'b01;
        alu_out = 6'b100110;
        alu_flag = 1;

        #20 $finish;
    end

    // Monitor signals
    initial begin
        $monitor("Time=%0t: clk=%b, reset=%b, start=%b, a=%d, b=%d,
op=%b, alu_in1=%d, alu_in2=%d, alu_op=%b, result=%d, flag=%b",
                $time, clk, reset, start, a, b, op, alu_in1,
alu_in2, alu_op, result, flag);
    end


endmodule

```


RTL Timing Diagram:

Check List: Have you added all the timing diagrams of ALU_TESTBENCH, CONTROLLER_TESTBENCH, TOP_TESTBENCH?	YES/NO
NB: Failing to add any required info will cause point penalty (1-2 Marks)	


alu_tb.v

 

controller_tb.v

 

top_tb.v

 

RTL Synthesis (130nm Skywater PDK with OpenLane toolchain):

Check List: Have you added *RTL synthesis summary*, *RTL synthesized design figure* and *Standard cell usage in synthesized design*?

YES

NB: Failing to add any required info will cause point penalty (1-2 Marks)

RTL synthesis summary

post_dff.rpt:

Metric	Count
Number of Wires	111
Number of wire bits	131
Number of public wires	10
Number of public wire bits	30
Number of ports	8
Number of port bits	24
Number of memories	0
Number of memory bits	0


Number of processes	0
Number of cells	114

stat.rpt:


Metric	Count
Number of Wires	63
Number of wire bits	79
Number of public wires	11
Number of public wire bits	27
Number of ports	8
Number of port bits	24
Number of memories	0
Number of memory bits	0
Number of processes	0
Number of cells	62

RTL synthesized design figure

Hierarchy.dot:

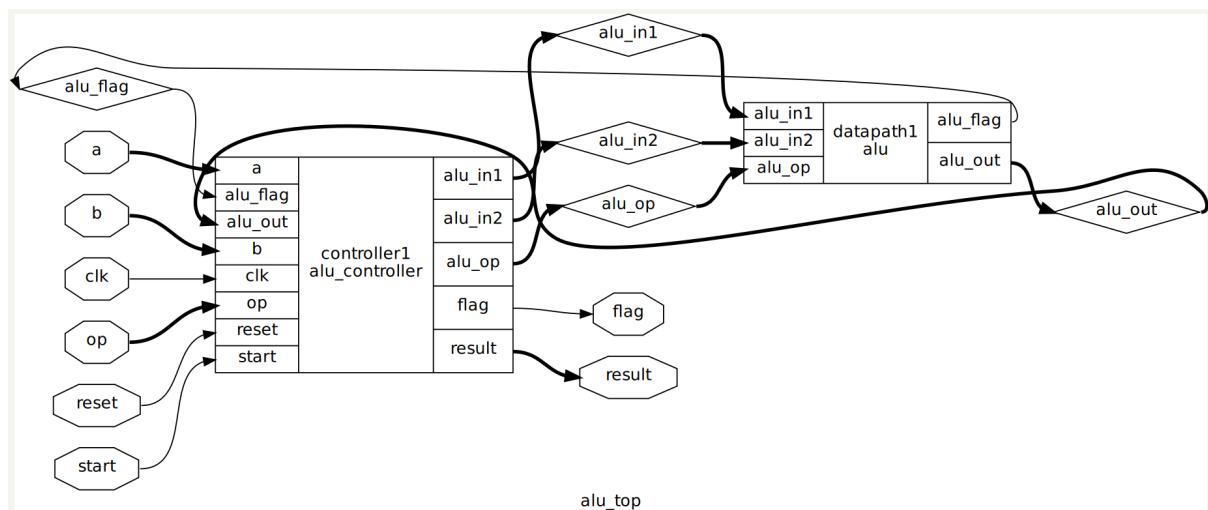

Primitive_techmap.dot:

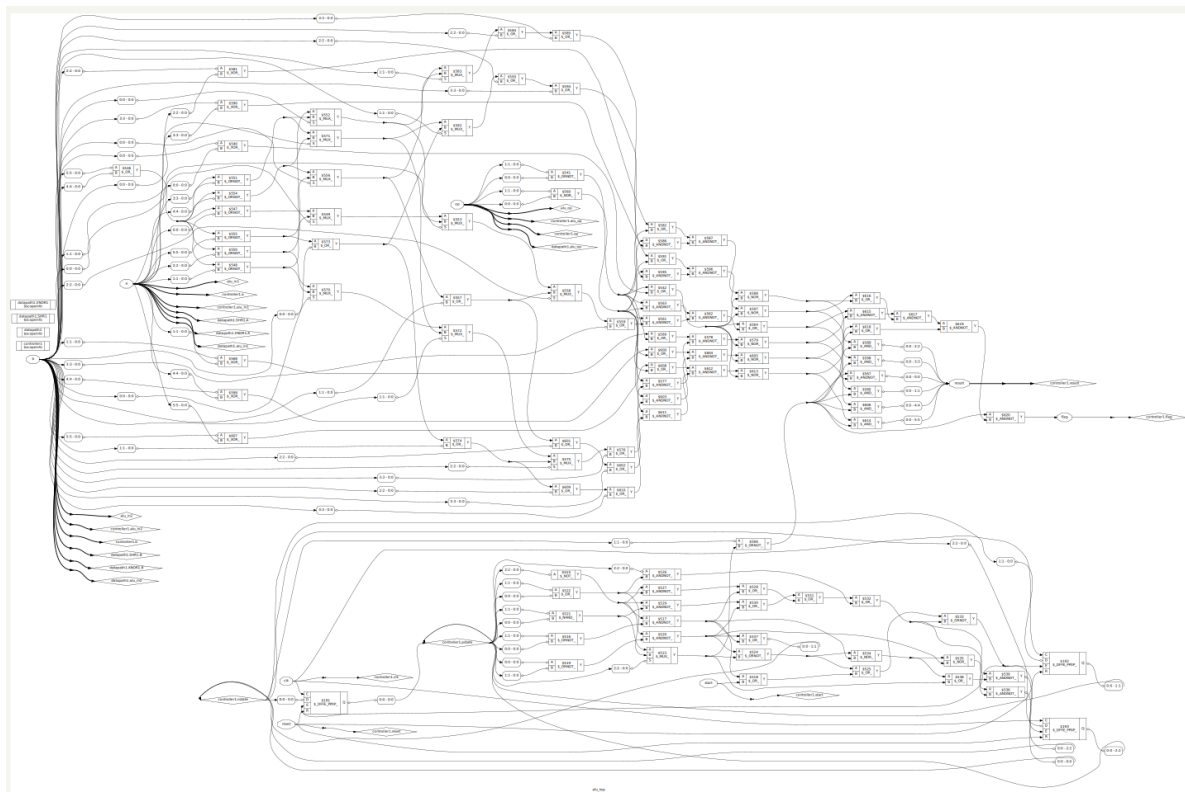

Standard cell usage in synthesized design

sky130_fd_sc_hd__a2111o_2	1
sky130_fd_sc_hd__a21o_2	1
sky130_fd_sc_hd__a21oi_2	8
sky130_fd_sc_hd__a2bb2o_2	2
sky130_fd_sc_hd__a31o_2	1
sky130_fd_sc_hd__and2_2	4
sky130_fd_sc_hd__and3_2	2
sky130_fd_sc_hd__and4b_2	1
sky130_fd_sc_hd__dfrrtp_2	3
sky130_fd_sc_hd__inv_2	6
sky130_fd_sc_hd__mux2_1	4
sky130_fd_sc_hd__nand2_2	1
sky130_fd_sc_hd__nand2b_2	1
sky130_fd_sc_hd__nor2_2	5
sky130_fd_sc_hd__o2111a_2	1
sky130_fd_sc_hd__o211ai_2	1
sky130_fd_sc_hd__o21a_2	3
sky130_fd_sc_hd__o21bai_2	1
sky130_fd_sc_hd__o22ai_2	1
sky130_fd_sc_hd__o32a_2	2
sky130_fd_sc_hd__or2_2	5
sky130_fd_sc_hd__or3_2	3
sky130_fd_sc_hd__or4b_2	1
sky130_fd_sc_hd__xor2_2	4

RTL Floorplan (130nm Skywater PDK with OpenLane toolchain)

Check List: Have you added RTL Floorplan info?	YES
NB: Failing to add any required info will cause point penalty (1-2 Marks)	

General RTL Floorplan Information		
Parameter	Value	Unit
Database Units(DBU)		--
Site Size	(2.72, 0.46)	µm
Die Area (BBox)	(0.0 0.0) to (49.705 60.425)	µm
Core Area(BBox)	(5.52 10.88) to (44.16 48.96)	µm
Core Area	1471.42	µm ²
Die Area	3003.42	µm ²
Placement Utilization		%

Openroad_floorplan.log:

```
Reading design constraints file at '/nix/store/b5k0h8cjlpydp7lb98p9n8qqanyralc-python3-3.11.9-env/lib/python3.11/site-packages/openlane/scripts/base.sdc$
[WARNING] No CLOCK_PORT found. A dummy clock will be used.
[WARNING STA-0366] port '__VIRTUAL_CLK__' not found.
[INFO] Using clock __VIRTUAL_CLK__...
[INFO] Setting output delay to: 2.0
[INFO] Setting input delay to: 2.0
[WARNING STA-0366] port '__VIRTUAL_CLK__' not found.
[INFO] Setting load to: 0.033442
[INFO] Setting clock uncertainty to: 0.25
[INFO] Setting clock transition to: 0.14999999999999994488848768742172978818416595458984375
[WARNING STA-0419] transition time can not be specified for virtual clocks.
[INFO] Setting timing derate to: 5%
[WARNING STA-0450] virtual clock __VIRTUAL_CLK__ can not be propagated.
Using site height: 2.72 and site width: 0.46...
[INFO] Using relative sizing for the floorplan.
[INFO IFP-0001] Added 14 rows of 84 site unithd.
[INFO IFP-0030] Inserted 0 tiecells using sky130_fd_sc_hd__conb_1/L0.
[INFO IFP-0030] Inserted 0 tiecells using sky130_fd_sc_hd__conb_1/HI.
[INFO] Extracting DIE_AREA and CORE_AREA from the floorplan
[INFO] Floorplanned on a die area of 0.0 0.0 49.705 60.425 (µm).
[INFO] Floorplanned on a core area of 5.52 10.88 44.16 48.96 (µm).
Writing metric design__die__bbox: 0.0 0.0 49.705 60.425
Writing metric design__core__bbox: 5.52 10.88 44.16 48.96
Setting global connections for newly added cells...
[INFO] Setting global connections...
Updating metrics...
Cell type report:
      Count      Area
Inverter          6    22.52
Sequential cell    3    78.83
Multi-Input combinational cell  53   496.73
Total             62   598.07
```

Or_metrix_out.json:

```
"design__die__bbox": "0.0 0.0 49.705 60.425",
"design__core__bbox": "5.52 10.88 44.16 48.96",
"design__io": 24,
"design__die__area": 3003.42,
"design__core__area": 1471.41,
"design__instance__count": 62,
"design__instance__area": 598.074,
"design__instance__count__stdcell": 62,
"design__instance__area__stdcell": 598.074,
"design__instance__count__macros": 0,
"design__instance__area__macros": 0,
"design__instance__utilization": 0.406463,
"design__instance__utilization__stdcell": 0.406463,
"design__instance__count__class:inverter": 6,
"design__instance__count__class:sequential_cell": 3,
"design__instance__count__class:multi_input_combinational_cell": 53,
"flow__warnings__count": 6,
"flow__errors__count": 0
```

RTL Power Analysis (130nm Skywater PDK with OpenLane toolchain)

Check List: Have you added RTL Power Analysis info?	YES
NB: Failing to add any required info will cause point penalty (1-2 Marks)	

```
=====
report_power
=====
===== nom_tt_025C_1v80 Corner =====
```

Group	Internal Power	Switching Power	Leakage Power	Total Power (Watts)	
Sequential	5.102053e-06	4.209583e-06	3.768916e-11	9.311674e-06	16.4%
Combinational	1.747334e-05	3.005282e-05	2.372030e-10	4.752640e-05	83.6%
Clock	0.000000e+00	0.000000e+00	2.203231e-10	2.203231e-10	0.0%
Macro	0.000000e+00	0.000000e+00	0.000000e+00	0.000000e+00	0.0%
Pad	0.000000e+00	0.000000e+00	0.000000e+00	0.000000e+00	0.0%

Total	2.257540e-05	3.426240e-05	4.952152e-10	5.683830e-05	100.0%
	39.7%	60.3%	0.0%		

GDS Layout (130nm Skywater PDK with OpenLane toolchain)

Check List: Have you added the GDS Layout figure?	YES
NB: Failing to add any required info will cause point penalty (1-2 Marks)	

